

Phyz Examples: Electric Current & Circuits

Physical Quantities • Symbols • Units • Brief Definitions

Charge • q or Q • coulomb [*KOO lom*]: C • A characteristic of certain fundamental particles.

Current • I • coulomb per second: C/s or ampere: A • The rate at which electric charge flows.

Voltage • V or \mathcal{E} • joule per coulomb: J/C or volt: V • Electric potential energy per unit of charge; electric “oomph.”

Resistance • R • volt per amp: V/A or ohm: Ω • A measure of the obstruction to flow of electric charge that a *body* possesses.

Power • P • watt: W • The rate at which energy is transferred in an electric circuit.

Equations

$$I = q/t \text{ • current} = \text{charge} / \text{time}$$

$$I = V/R \text{ or } \mathcal{E}/R \text{ • Ohm's Law • current} = \text{voltage} / \text{resistance}$$

$$P = IV \text{ or } I\mathcal{E} \text{ • Joule's Law • power} = \text{current} \cdot \text{voltage}$$

$$P = I^2R \text{ • power} = \text{square of current} \cdot \text{resistance}$$

$$P = V^2/R \text{ or } \mathcal{E}^2/R \text{ • power} = \text{square of voltage} / \text{resistance}$$

Smooth Operations Examples

1. What is the current in a wire if 15.7 C of charge move past a point in the wire every 2.3 s?

$$1. q = 15.7 \text{ C} \quad t = 2.3 \text{ s} \quad I = ?$$

$$I = q/t$$

$$I = 15.7 \text{ C} / 2.3 \text{ s}$$

$$I = \underline{6.8 \text{ A}}$$

2. A current of 0.82 A passes through a 47- Ω resistor. What is the potential difference across the resistor?

(The question is asking for the voltage.)

$$2. I = 0.82 \text{ A} \quad R = 47 \Omega \quad V = ?$$

$$I = V/R$$

$$V = IR$$

$$V = 0.82 \text{ A} \cdot 47 \Omega$$

$$V = \underline{39 \text{ V}}$$

3. If a 100-W stereo system is plugged into the 120-V line voltage used in US homes, how much current does it draw?

$$3. P = 100 \text{ W} \quad V = 120 \text{ V} \quad I = ?$$

$$P = IV$$

$$I = P/V$$

$$I = 100 \text{ W} / 120 \text{ V}$$

$$I = \underline{0.83 \text{ A}}$$

4. What is the resistance of a 1500-W hair dryer that draws 13 A of current?

$$4. P = 1500 \text{ W} \quad I = 13 \text{ A} \quad R = ?$$

$$P = I^2R$$

$$R = P/I^2$$

$$R = 1500 \text{ W} / (13 \text{ A})^2$$

$$R = \underline{8.9 \Omega}$$

5. An appliance with a resistance of 36 Ω operates at 9.0 V. At what rate does it dissipate energy? (That is, what's the power?)

$$5. R = 36 \Omega \quad V = 9.0 \text{ V} \quad P = ?$$

$$P = V^2/R$$

$$P = (9.0 \text{ V})^2 / 36 \Omega$$

$$P = \underline{2.3 \text{ W}}$$

6. How much voltage must be applied to an 8- Ω resistor to produce 27 W of power?

$$6. P = 27 \text{ W} \quad R = 8 \Omega \quad V = ?$$

$$P = V^2/R$$

$$V = \sqrt{PR}$$

$$V = \sqrt{(27 \text{ W} \cdot 8 \Omega)}$$

$$V = \underline{15 \text{ V}}$$

Equations from combining Ohm's Law and Joule's Law

Complete all the petals of the flower by rearranging $I = V/R$, $P = IV$, $P = I^2R$, and $P = V^2/R$.

