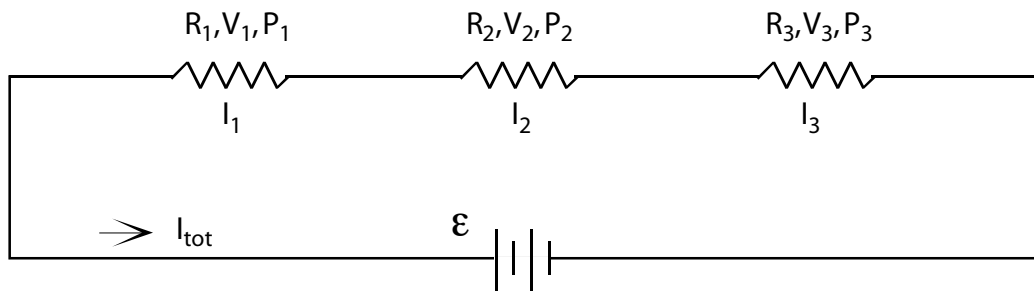


# Phyz Examples: Series Circuits



In ALL circuits...

$$I_{tot} = \frac{\epsilon}{R_{eq}}$$

## OHM'S LAW

The total current in the circuit is equal to the emf of the voltage source (battery) divided by the equivalent resistance of the circuit.

$$P_{tot} = I_{tot}\epsilon$$

## JOULE'S LAW

The total power developed in the circuit is equal to the product of the total current and the emf of the voltage source.

$$P_{tot} = P_1 + P_2 + P_3 + \dots$$

## POWER SUM

The total power in the circuit is equal to sum of the power values of each of the resistors.

In SERIES circuits...

$$I_{tot} = I_1 = I_2 = I_3 = \dots$$

## SERIES CURRENT

The current in a series circuit is the same in all elements of the circuit.

$$\epsilon = V_1 + V_2 + V_3 + \dots$$

## SERIES VOLTAGE

The voltage in a series circuit is divided among the resistors. The potential of the battery is equal to the sum of the potentials across each resistor.

$$R_{eq} = R_1 + R_2 + R_3 + \dots$$

## SERIES EQUIVALENT RESISTANCE

The equivalent resistance of a series circuit is equal to the sum of the resistance values of each resistor.


In ANY resistor R<sub>n</sub>...

$$V_n = I_n R_n$$

$$P_n = I_n V_n$$

$$P_n = V_n^2 / R_n$$

$$P_n = I_n^2 R_n$$

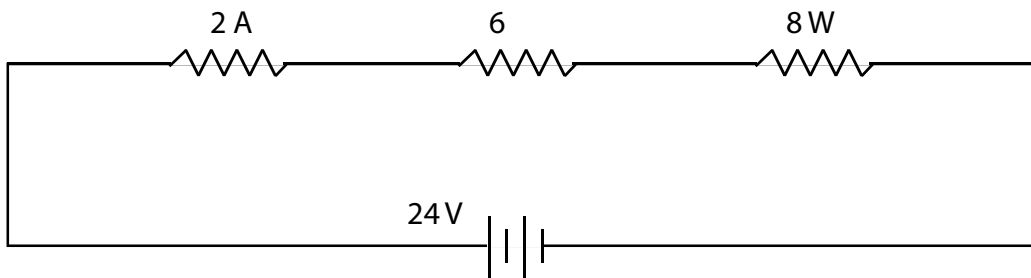

Given this information, what can be determined about the circuit? EVERYTHING!!!

1. Since the total potential in the circuit is 24 V and the current in the circuit is 2 A, the equivalent resistance in the circuit is

$$R_{eq} = \varepsilon/I = 24 \text{ V} / 2 \text{ A} = 12 \Omega$$

2. Since  $R_2 = 6 \Omega$  and  $I = 2 \text{ A}$ , the potential across  $R_2$  is

$$V_2 = IR_2 = 2 \text{ A} \cdot 6 \Omega = 12 \text{ V}$$

3. The power dissipated in  $R_2$  is

$$P_2 = I^2 R_2 = (2 \text{ A})^2 \cdot 6 \Omega = 24 \text{ W}$$

4. Since the power dissipated in  $R_3$  is 8 W, the potential drop across  $R_3$  is

$$V_3 = P_3/I = 8 \text{ W} / 2 \text{ A} = 4 \text{ V}$$

5. And the resistance of  $R_3$  is

$$R_3 = P/I^2 = 8 \text{ W} / (2 \text{ A})^2 = 2 \Omega$$

6. Since the equivalent resistance is 12  $\Omega$ ,  $R_2$  is 6  $\Omega$ , and  $R_3$  is 2  $\Omega$ ,

$$R_1 = R_{eq} - R_2 - R_3 = 12 \Omega - 6 \Omega - 2 \Omega = 4 \Omega$$

7. The potential drop across  $R_1$  is

$$V_1 = \varepsilon - V_2 - V_3 = 24 \text{ V} - 12 \text{ V} - 4 \text{ V} = 8 \text{ V} \quad \text{or} \quad V_1 = IR_1 = 2 \text{ A} \cdot 4 \Omega = 8 \text{ V}$$

8. And so the power dissipated in  $R_1$  is

$$P_1 = I^2 R_1 = (2 \text{ A})^2 \cdot 4 \Omega = 16 \text{ W}$$

9. So the total power dissipated in the circuit is

$$P_{tot} = P_1 + P_2 + P_3 = 16 \text{ W} + 24 \text{ W} + 8 \text{ W} = 48 \text{ W} \quad \text{or} \quad P_{tot} = I\varepsilon = 2 \text{ A} \cdot 24 \text{ V} = 48 \text{ W}$$