Prelab Phyzjob: Haleh Cow! Complete before the logic Gates Phyzlab




This exercise is designed to guide you through the subtle points of AND and OR gate Boolean logic. You will find it helpful on sections 1-7 of the Logic Gates Lab. (students Haleh Partovi and Jay Draeger found this exercise very helpful.) It will **not** help you discover the design of the NOT gate.

We have a cow, Besse, that hopes to get to her pasture (marked with a star) to graze. Your challenge is to write the minimum conditions that must be met for Besse to get to her pasture. Consider case 1 shown to the right.

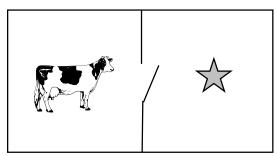
1. Single gate

IF the gate is open, THEN Besse can get through. If the gate is closed, Besse cannot get to her pasture. We call this an IF-THEN gate. The cases below also include a table to be completed. The table lists all possible combinations of open/closed gates and the corresponding results for the gate configuration under consideration.



Now consider the following situations. Cases 2 and 3 have been completed for you. Complete cases 4–7 by filling in the truth table, writing the descriptive statement, or sketching an appropriate pasture diagram.


2. Two gates in a row

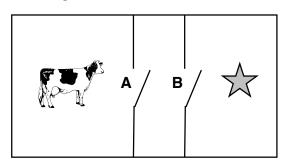

Besse can get to pasture only if gate A AND gate B are open.

A open	B open	Graze?
no	no	no
no	yes	no
yes	no	no
yes	yes	yes

3. Two gates side by side

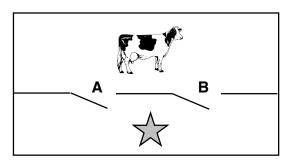

Besse can get to pasture only if gate A OR gate B is open.

A open	B open	Graze?
no	no	no
no	yes	yes
yes	no	yes
yes	yes	yes


nueur:

Please complete the **other** side of this sheet before reading this note.

The cow's gates are analogous to our switches. But a word of caution: The cow can pass through a gate if the gate is OPEN; current can pass through a switch only if the switch is CLOSED! A closed gate is to the cow what an open switch is to electric


READ AFTER COMPLETING THE JOB AND BEFORE GOING TO THE LAB

4. Three gates in a row

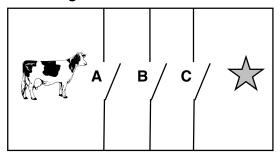

A open	B open	C open	Graze?
no	no	no	
no	no	yes	
по	yes	по	
no	yes	yes	
yes	no	по	
yes	no	yes	
yes	yes	по	
yes	yes	yes	

6. Three Gate Combo Alpha

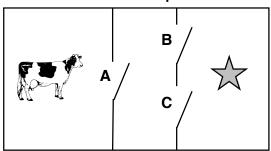

A open	B open	C open	Graze?
no	no	no	no
no	no	yes	no
no	yes	no	no
no	yes	yes	no
yes	no	no	no
yes	по	yes	yes
yes	yes	по	yes
yes	yes	yes	yes

5. Three gates side k	ov sid	е
------------------------------	--------	---



Besse can get to pasture only if gate A OR gate B OR gate C is open.

A open	B open	C open	Graze?
no	no	no	no
no	no	yes	yes
по	yes	no	yes
по	yes	yes	yes
yes	по	по	yes
yes	по	yes	yes
yes	yes	по	yes
yes	yes	yes	yes

7. Three Gate Combo Beta



Besse can get to pasture only if gate A OR gate B AND gate C is open.

A open	B open	C open	Graze?
no	no	no	
no	no	yes	
no	yes	no	
no	yes	yes	
yes	no	no	
yes	no	yes	
yes	yes	no	
yes	yes	yes	