


# PhyzJob: Circuit Puzzles

## CONCEPTS AND NUMBERS


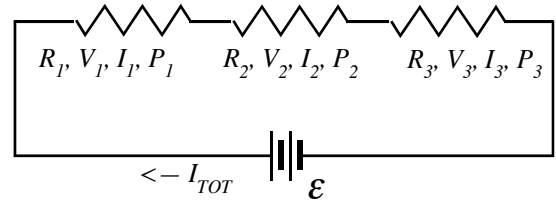
### SERIES INQUIRIES (Items 1–5)

Consider the series circuit shown to the right.



1. If  $I_1 = 3.7$  A, what is

a.  $I_2$ ? \_\_\_\_\_ b.  $I_3$ ? \_\_\_\_\_

c.  $I_{TOT}$ ? \_\_\_\_\_

2. If  $V_1 = 2$  V,  $V_2 = 1$  V, and  $V_3 = 5$  V, what is  $\epsilon$ ? \_\_\_\_\_

3. If  $V_1 = V_2 = V_3 = 4$  V and  $I_1 = I_2 = I_3 = 3$  A, what is

a.  $\epsilon =$  \_\_\_\_\_ b.  $I_{TOT}$ ? \_\_\_\_\_

4. If  $\epsilon = 18$  V,  $V_1 = 4$  V, and  $V_2 = 8$  V, what is  $V_3$ ? \_\_\_\_\_

5. If  $I_1 = 5$  A,  $R_2 = 3$   $\Omega$ , and  $P_3 = 10$  W, what is


a.  $V_2$ ? \_\_\_\_\_ b.  $V_3$ ? \_\_\_\_\_

c.  $P_2$ ? \_\_\_\_\_

d.  $R_3$ ? \_\_\_\_\_
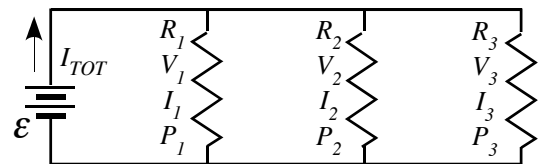
### PARALLEL PONDERABLES (Items 6–9)

Consider the parallel circuit shown to the right.



6. If  $\epsilon = 7.3$  V, what is

a.  $V_1$ ? \_\_\_\_\_ b.  $V_2$ ? \_\_\_\_\_

c.  $V_3$ ? \_\_\_\_\_

7. If  $I_1 = 3.4$  A,  $I_2 = 1.8$  A, and  $I_3 = 0.6$  A, what is  $I_{TOT}$ ? \_\_\_\_\_

8. If  $V_1 = V_2 = V_3 = 4$  V and  $I_1 = I_2 = I_3 = 3$  A, what is

a.  $\epsilon =$  \_\_\_\_\_ b.  $I_{TOT}$ ? \_\_\_\_\_

