


PhyzJob: Series Circuits NUMBER PUZZLES

Felix

Apply Ohm's law, Joule's law, and your understanding of the nature of series circuits to solve the numerical problems that follow.

Ex. If $\mathcal{E} = 12 \text{ V}$, $R_1 = 3.0 \ \Omega$ and $R_2 = 6.0 \ \Omega$, what is

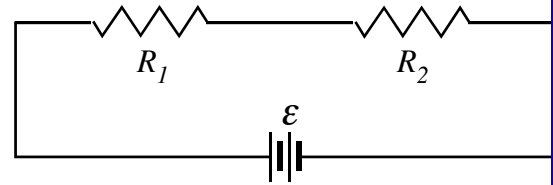- the equivalent resistance of the circuit?
- the total current in the circuit?
- the power dissipated in R_1 ?
- the voltage across R_2 ?



a. $R_{EQ} = R_1 + R_2$ (for series circuit)
 $R_{EQ} = 3.0 \ \Omega + 6.0 \ \Omega$
 $R_{EQ} = 9.0 \ \Omega$


b. $I = \mathcal{E}/R_{EQ}$
 $I = 12 \text{ V} / 9.0 \ \Omega$
 $I = 1.3 \text{ A}$

c. $P_1 = I^2 R_1$
 $P_1 = (1.3 \text{ A})^2 \cdot 3.0 \ \Omega$
 $P_1 = 5.1 \text{ W}$

d. $V_2 = IR_2$
 $V_2 = 1.3 \text{ A} \cdot 6.0 \ \Omega$
 $V_2 = 8.0 \text{ V}$

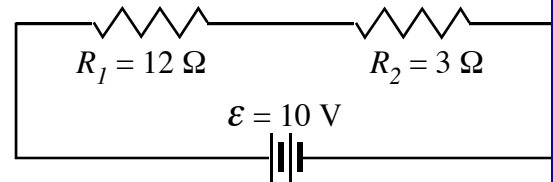1. If $\mathcal{E} = 10 \text{ V}$, $R_1 = 12 \ \Omega$ and $R_2 = 3.0 \ \Omega$, what is

- the equivalent resistance of the circuit?
- the total current in the circuit?
- the power dissipated in R_1 ?
- the voltage across R_2 ?




a. $R_{EQ} = R_1 + R_2$ (for series circuit)
 $R_{EQ} = 12 \ \Omega + 3.0 \ \Omega$
 $R_{EQ} = 15 \ \Omega$

b. $I = \mathcal{E}/R_{EQ}$
 $I = 10 \text{ V} / 15 \ \Omega$
 $I = 0.67 \text{ A}$

c. $P_1 = I^2 R_1$
 $P_1 = (0.67 \text{ A})^2 \cdot 12 \ \Omega$
 $P_1 = 5.4 \text{ W}$

d. $V_2 = IR_2$
 $V_2 = 0.67 \text{ A} \cdot 3 \ \Omega$
 $V_2 = 2.0 \text{ V}$

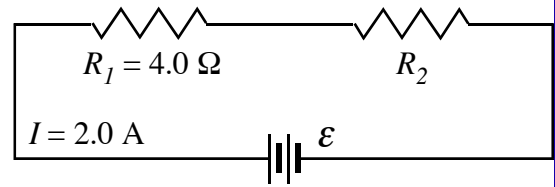2. If $I = 2.0 \text{ A}$, $R_1 = 4.0 \Omega$, and $V_2 = 5.0 \text{ V}$, what is
- the voltage across R_1 ?
 - the resistance of R_2 ?
 - the power dissipated in the circuit?
 - the voltage of the battery?



a. $V_1 = IR_1$
 $V_1 = 2.0 \text{ A} \cdot 4.0 \Omega$
 $V_1 = 8.0 \text{ V}$

b. $R_2 = V_2/I$
 $R_2 = 5.0 \text{ V} / 2.0 \text{ A}$
 $R_2 = 2.5 \Omega$

c. $P_{\text{TOT}} = I^2 R_{\text{EQ}}$
 $P_{\text{TOT}} = (2.0 \text{ A})^2 (4 \Omega + 2.5 \Omega)$
 $P_{\text{TOT}} = 26 \text{ W}$

d. $\epsilon = IR_{\text{EQ}}$
 $\epsilon = 2.0 \text{ A} \cdot (4 \Omega + 2.5 \Omega)$
 $\epsilon = 13 \text{ V}$

3. If $\epsilon = 24 \text{ V}$, $R_1 = 8.0 \Omega$, and $R_2 = 6.0 \Omega$, what is the current through R_2 ?

$I = \epsilon/R_{\text{EQ}}$
 $I = 24 \text{ V} / (8 \Omega + 6 \Omega)$
 $I = 1.7 \text{ A}$

4. If $\epsilon = 9.0 \text{ V}$, $R_1 = 5.0 \Omega$, and $R_2 = 13 \Omega$, what is the power dissipated in the circuit?

$P_{\text{TOT}} = \epsilon^2/R_{\text{EQ}}$
 $P_{\text{TOT}} = (9 \text{ V})^2 / (5 \Omega + 13 \Omega)$
 $P_{\text{TOT}} = 4.5 \text{ W}$

5. If $I = 0.75 \text{ A}$, $R_1 = 6 \Omega$, and $R_2 = 15 \Omega$, what is the voltage

- across R_1 ?
- across R_2 ?
- of the battery?

a. $V_1 = IR_1 = 0.75 \text{ A} \cdot 6 \Omega = 4.5 \text{ V}$

b. $V_2 = IR_2 = 0.75 \text{ A} \cdot 15 \Omega = 11.3 \text{ V}$

c. $\epsilon = V_1 + V_2 = 4.5 \text{ V} + 11.3 \text{ V} = 15.8 \text{ V}$